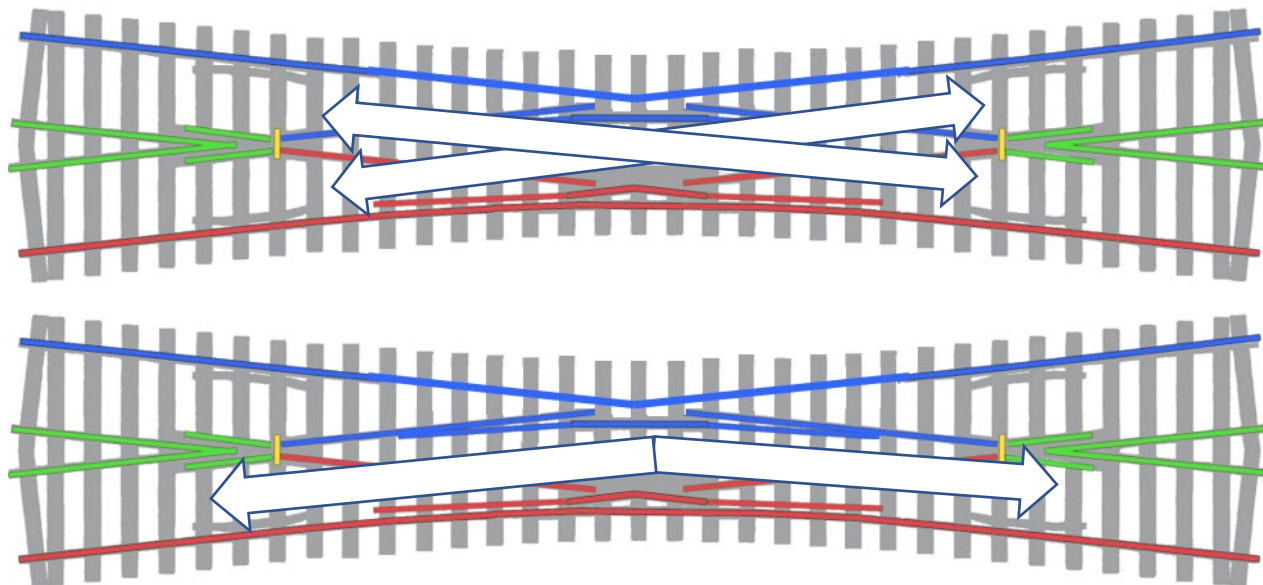





Wiring a Peco Single Slip for Cobalt iP Digitals


Mechanically, there are two scenarios: "diamond" and "slip".



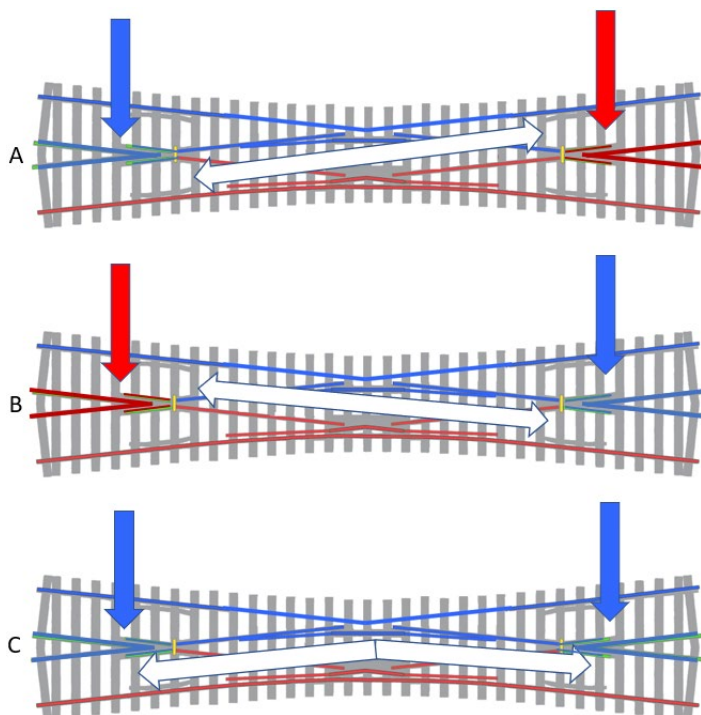However, on a 2-rail electric model railway, in order to achieve correct frog polarity there are three turnout position scenarios to do this.






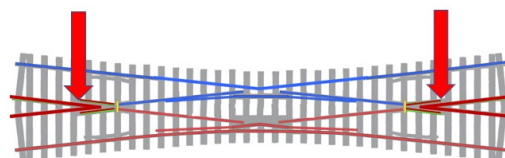
A fourth turnout position will cause an electrical conflict and so should not be used.



Originally drawn for Pete R




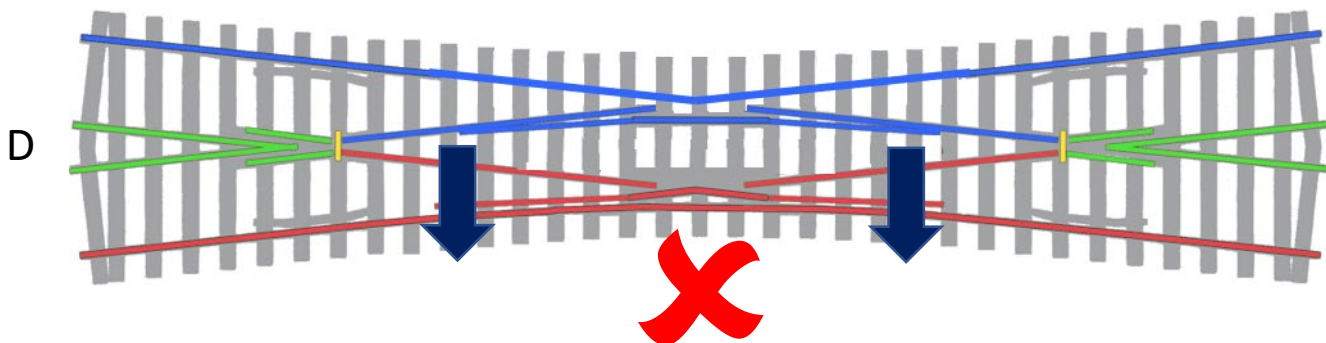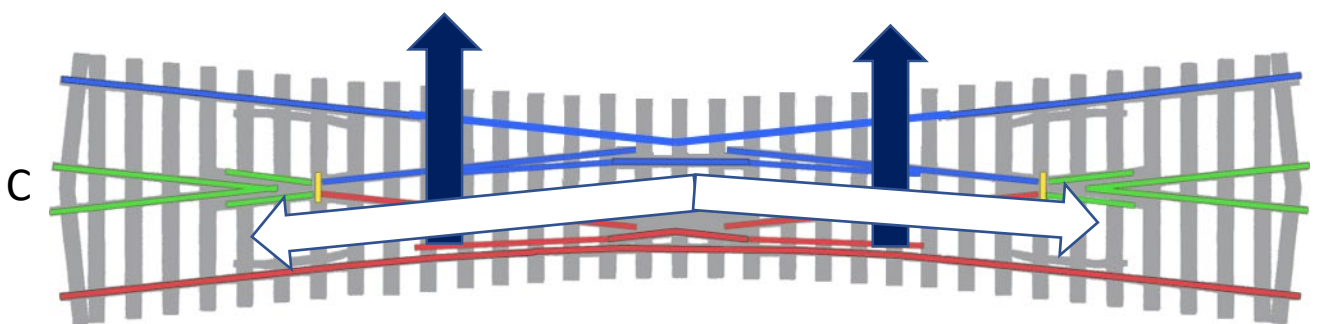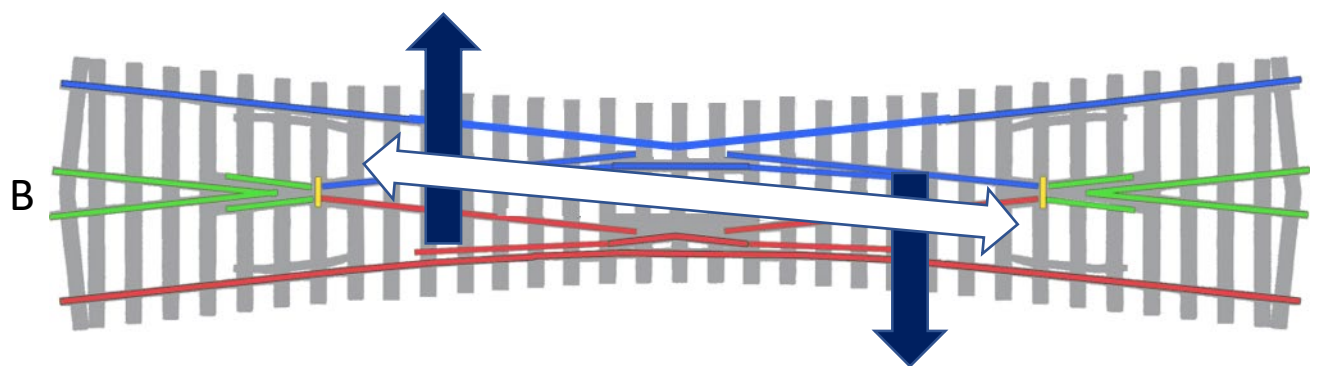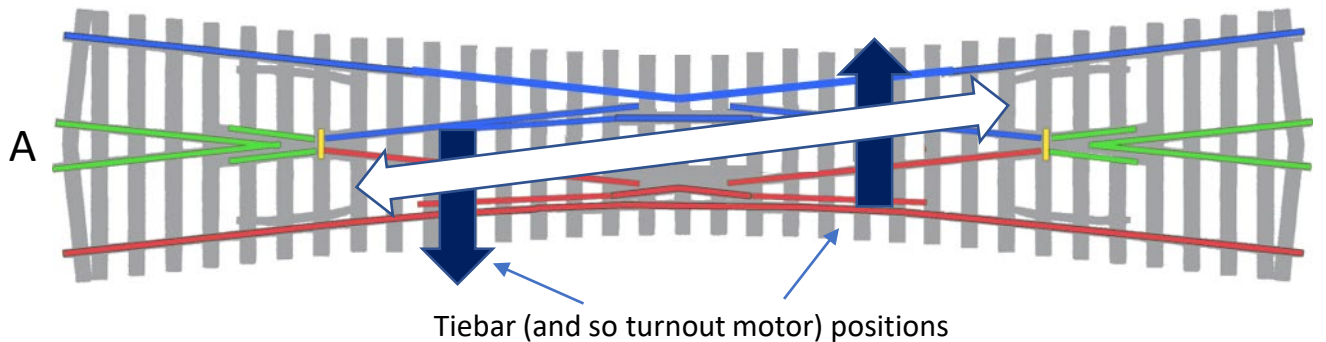Wiring a Peco Single Slip for Cobalt iP Digitals





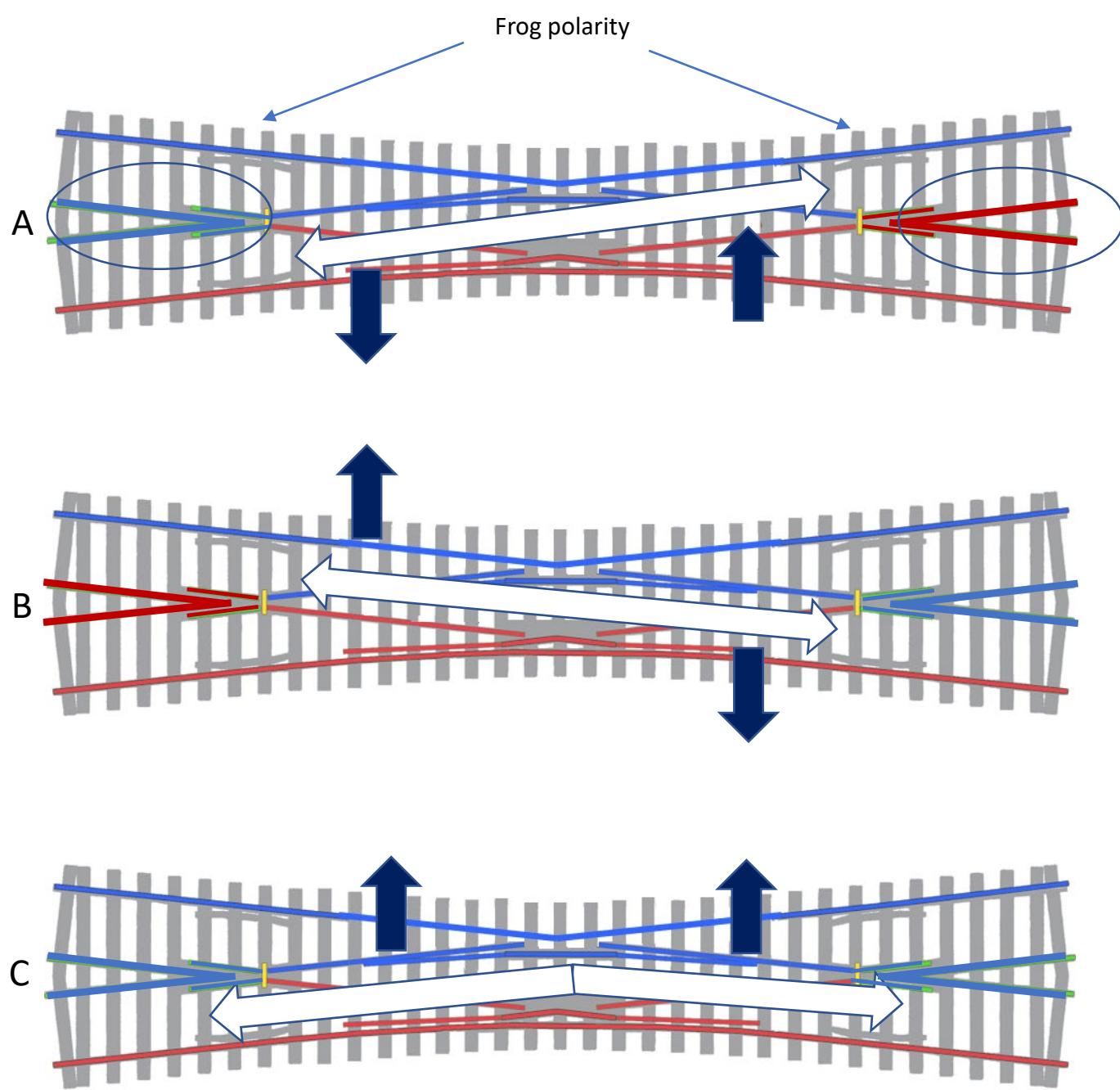
Wiring a Peco Single Slip for Cobalt iP Digitals






Wiring a Peco Single Slip for Cobalt iP Digitals

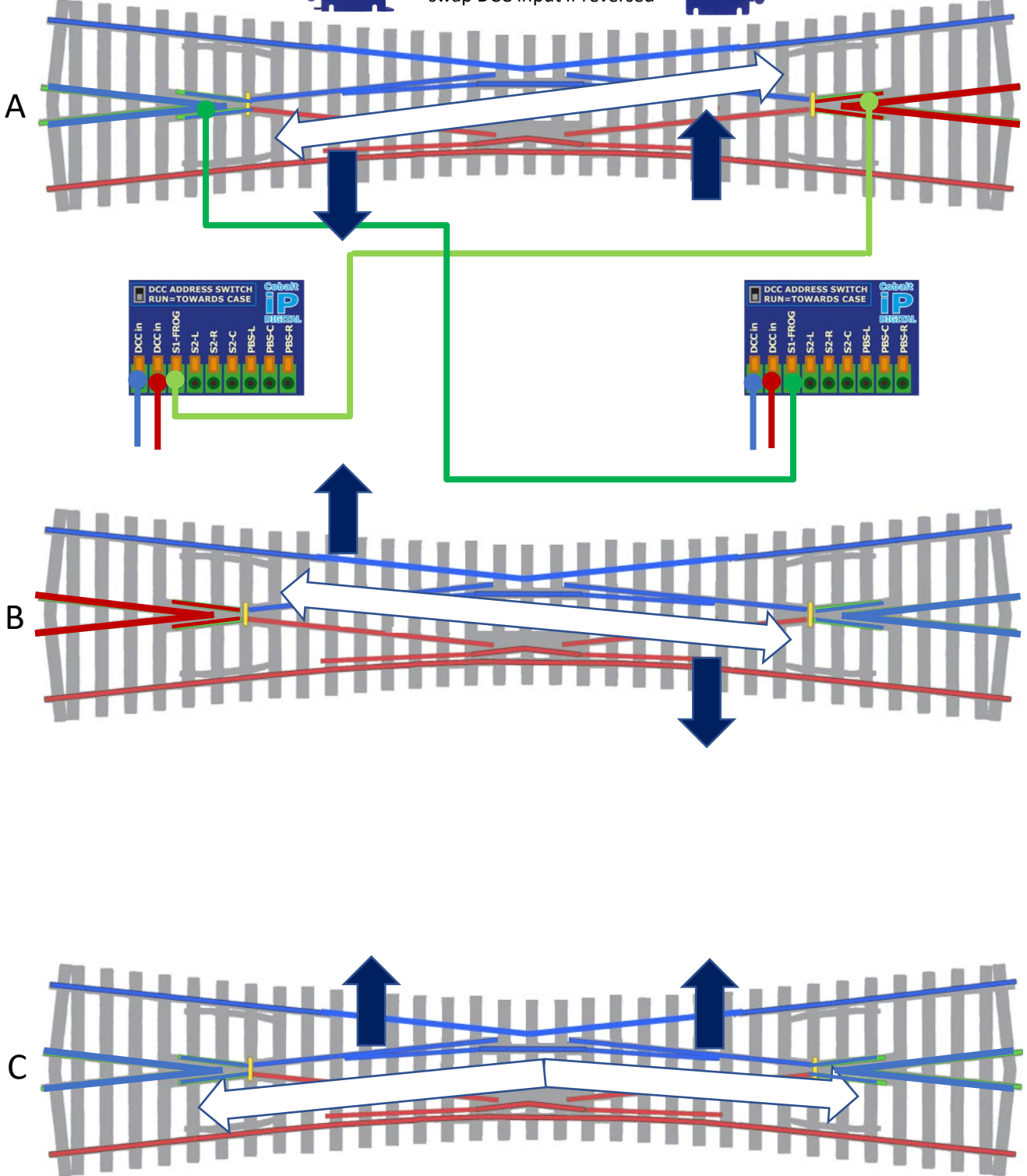Wiring is for this orientation
– swap DCC input if reversed








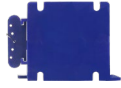Wiring a Peco Single Slip for Cobalt iP Digitals



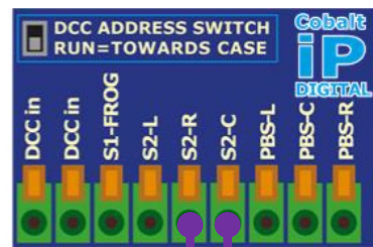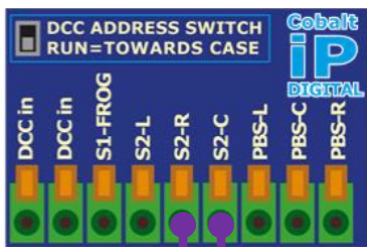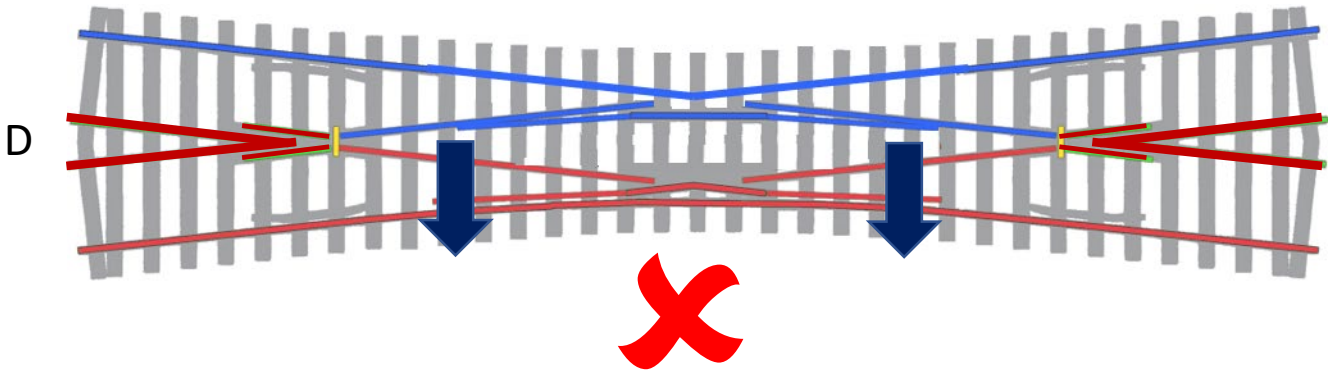Cobalt #1 can't throw "DOWN" if Cobalt #2 is "DOWN" and vice versa



Tip: Use this switching logic to feed a buzzer or an LED. Use S2-L if the Cobalt is oriented the other way.

