





# Cobalt Point Motor Switch Logic


## Cobalt iP Digital
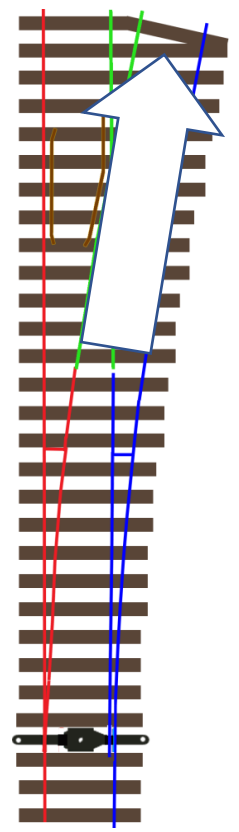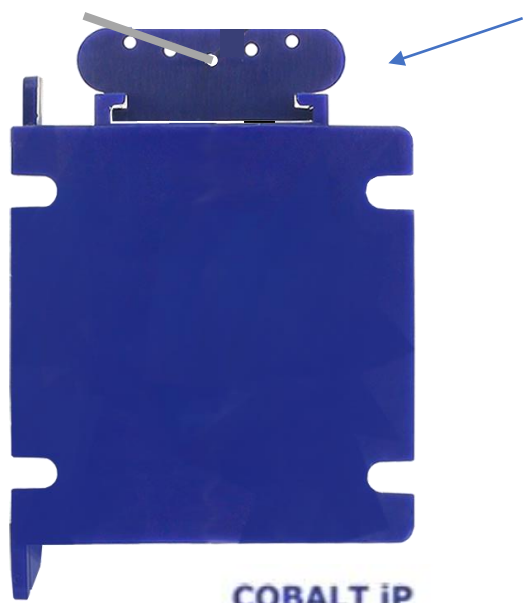
### Scenario:

- Looking down the spigot is to the right.
- The throw arm is to the left.
- The motor is fixed under the baseboard in this orientation...
- ..so... the turnout is switched to right.



COBALT iP  
DIGITAL

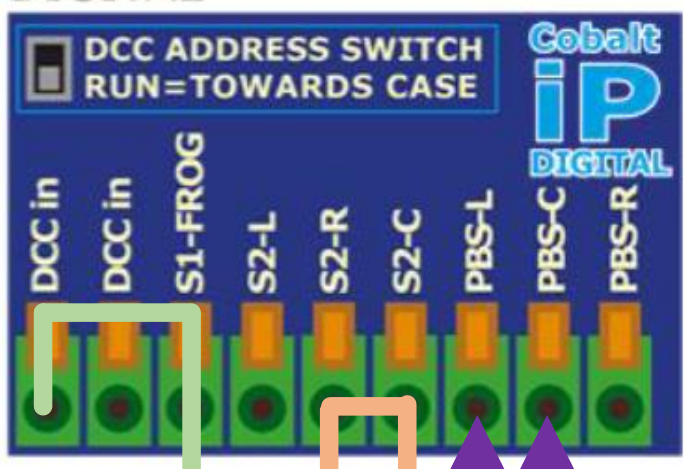

S1-Frog takes power from the **DCC In #1** i.e. the first connector.

S2-C connects to S2-R

Bridging PBS-C to PBS-L switches the turnout to the right (PBS-C to PBS-R switches it to left and PBS-L to PBS-R switches the motor left/right alternately). Reversing the motor (using address 197) will reverse this pushbutton rule.



## Cobalt Point Motor Switch Logic

### Cobalt iP (Analog)/Ω





For this motor position, **DC in** will be + and – as shown when this switch is set towards the body.

Note how different LEDs have different resistor values. These can be varied slightly for brightness and depend on the voltage across **DC in**. Do not start with too low a variation!
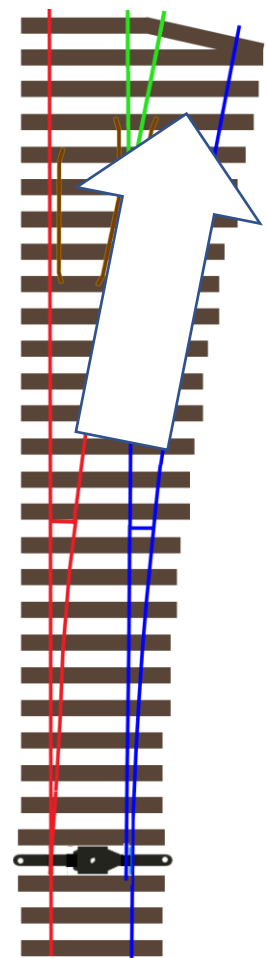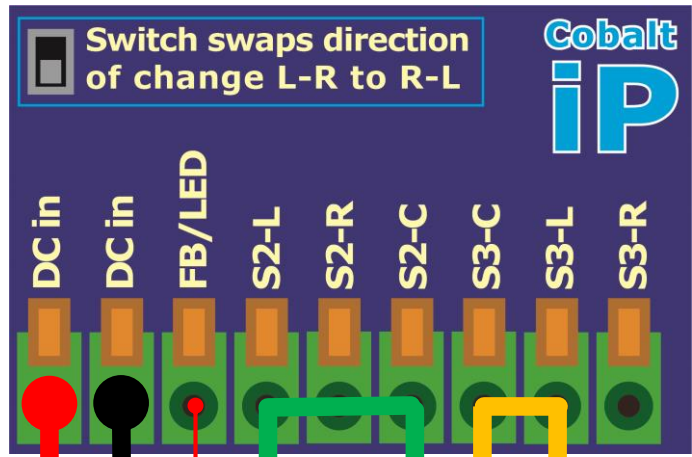
### Scenario:

- Looking down the spigot is to the right.
- The throw arm is to the left.
- The motor is fixed under the baseboard in this orientation..
- ..so... the turnout is switched to right.

Swapping direction with this switch on the Cobalt iP means **DC in #1** will now have to be “black” and **DC in #2** “red” to achieve this throw arm position. Consequently, the LEDs will be reversed i.e. the green LED will light instead.



S2 switches S2-C to S2-L

S3 switches S3-C to S3-L


Note how the S2 logic is opposite to the Cobalt iP Digital !




# Cobalt Point Motor Switch Logic
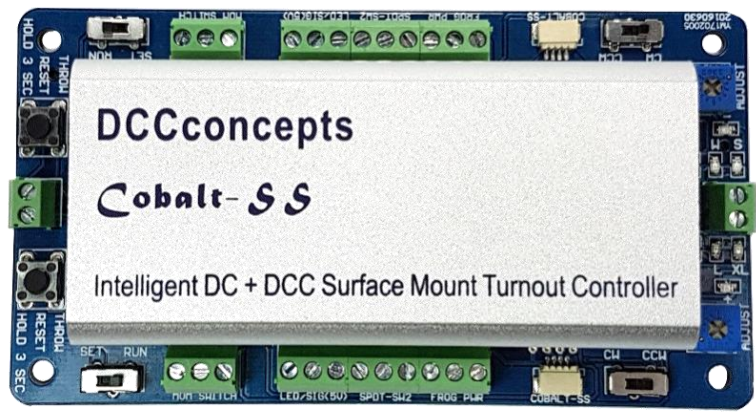
## Cobalt SS


This MOM SWITCH input (i.e. momentary push button switch input) assumes a setting of CW not CCW



Direction of throw

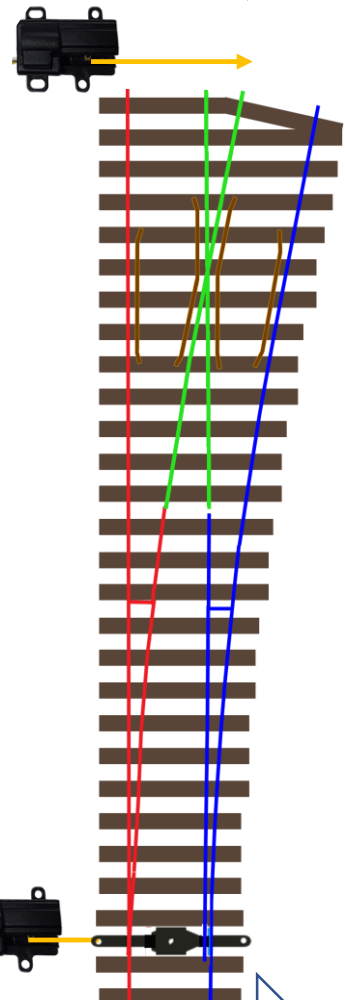

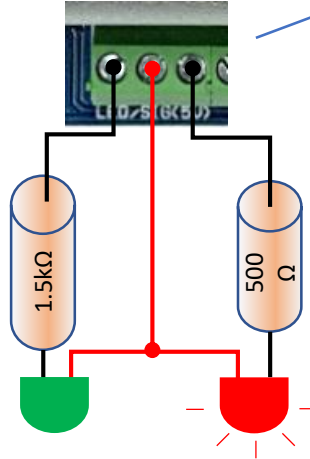When commanded to throw in the other direction, the central connector of LED/SIG(5V) remains at +5V but the left connector is now ground i.e. 'negative'.



The CW / CCW setting only affects input (including the MOM) but not the output switches (LED/SIG(5V), SPDT-SW2 and FROG PWR). Consider these outputs as if they are linked to the actual motor shaft movement. Unlike the Cobalt iP Digital, FROG PWR is a SPDT switch like SPDT-SW2, not a power output.



Direction of throw



Note how different LEDs have different resistor values. These values are indicative and can be varied (with caution) for brightness.